

Oct 15, 10 13:25 alu\_design.v Page 1/5

```

module proj2_testbench;
  wire [15:0] out;
  reg clk;
  reg [15:0] a, b;
  reg [2:0] OPCODE;
  wire Zero, Overflow;

  ALU16_CLA DUT(a, b, OPCODE, out, Zero, Overflow);

  always
    #5 clk = ~clk;

  // Initialize signals
  initial begin
    clk = 1'b0; //initialize clk value to 0 at t=0

    a = 16'b0000000000000001;
    b = 16'b0000000000000001;
    OPCODE = 3'b111;
  end

  //always @(posedge clk)
  // a = a + 2;
  //always @(posedge clk)
  //b = b + 1;
endmodule

//ALU using Ripple/Fulladder Modules://
module ALU_slice(a, b, Carry_In, Carry_Out, OPCODE, out, Less);
  input a,b,Carry_In, Less;
  input [2:0] OPCODE;
  output out, Carry_Out;
  wire AND, OR, SUM, binvert;
  reg temp_b;

  assign binvert = OPCODE[2];
  always @*
  begin
    temp_b = b;
    if (binvert == 1'b1)
      temp_b = ~b;
    end
    assign AND = a & temp_b;
    assign OR = a | temp_b;
    fulladder f0(a, temp_b, Carry_In, SUM, Carry_Out);
    mux4 f1(AND, OR, SUM, Less, OPCODE[1:0], out);
  endmodule

module ALU_slice_MSB(a, b, Carry_In, Overflow, OPCODE, out, set);
  input a,b,Carry_In;
  input [2:0] OPCODE;
  output Overflow, out, set;
  ALU_slice f0(a, b, Carry_In, Overflow, OPCODE, out, 1'b0);
  assign set = out;
endmodule

module ALU16(a, b, OPCODE, out, Zero, Overflow);
  input [15:0] a, b;
  input [2:0] OPCODE;
  output [15:0] out;
  output Zero, Overflow;
  wire [15:0] Carry;
  wire set;
  ALU_slice f00(a[0], b[0], OPCODE[2], Carry[0], OPCODE, out[0], set); //pass
  in Binvert as the carry
  ALU_slice f01(a[1], b[1], Carry[0], Carry[1], OPCODE, out[1], 1'b0);
  ALU_slice f02(a[2], b[2], Carry[1], Carry[2], OPCODE, out[2], 1'b0);
  ALU_slice f03(a[3], b[3], Carry[2], Carry[3], OPCODE, out[3], 1'b0);

```

Oct 15, 10 13:25 alu\_design.v Page 2/5

```

  ALU_slice f04(a[4], b[4], Carry[3], Carry[4], OPCODE, out[4], 1'b0);
  ALU_slice f05(a[5], b[5], Carry[4], Carry[5], OPCODE, out[5], 1'b0);
  ALU_slice f06(a[6], b[6], Carry[5], Carry[6], OPCODE, out[6], 1'b0);
  ALU_slice f07(a[7], b[7], Carry[6], Carry[7], OPCODE, out[7], 1'b0);
  ALU_slice f08(a[8], b[8], Carry[7], Carry[8], OPCODE, out[8], 1'b0);
  ALU_slice f09(a[9], b[9], Carry[8], Carry[9], OPCODE, out[9], 1'b0);
  ALU_slice f10(a[10], b[10], Carry[9], Carry[10], OPCODE, out[10], 1'b0);
  ALU_slice f11(a[11], b[11], Carry[10], Carry[11], OPCODE, out[11], 1'b0);
  ALU_slice f12(a[12], b[12], Carry[11], Carry[12], OPCODE, out[12], 1'b0);
  ALU_slice f13(a[13], b[13], Carry[12], Carry[13], OPCODE, out[13], 1'b0);
  ALU_slice f14(a[14], b[14], Carry[13], Carry[14], OPCODE, out[14], 1'b0);
  ALU_slice_MSB f15(a[15], b[15], Carry[14], Carry[15], OPCODE, out[15], set);
  assign Zero = (out==16'h0000);
  assign Overflow = Carry[15];
endmodule

//ALU Carry Look Ahead Modules://
module ALU_slice_CLA(a, b, Carry_In, Carry_Out, OPCODE, out, Less);
  input [3:0] a,b,Less;
  input Carry_In;
  input [2:0] OPCODE;
  output [3:0] out;
  output Carry_Out;
  wire [3:0] AND, OR, SUM;
  wire binvert;
  reg [3:0] temp_b;

  assign binvert = OPCODE[2];
  always @*
  begin
    temp_b = b;
    if (binvert == 1'b1)
      temp_b = ~b;
    end
    assign AND = a & temp_b;
    assign OR = a | temp_b;
    ripple_adder_LA f0(a, temp_b, Carry_In, Carry_Out, SUM);

    mux4 f1(AND[0], OR[0], SUM[0], Less[0], OPCODE[1:0], out[0]);
    mux4 f2(AND[1], OR[1], SUM[1], Less[1], OPCODE[1:0], out[1]);
    mux4 f3(AND[2], OR[2], SUM[2], Less[2], OPCODE[1:0], out[2]);
    mux4 f4(AND[3], OR[3], SUM[3], Less[3], OPCODE[1:0], out[3]);
  endmodule

module ALU_slice_CLA_MSB(a, b, Carry_In, Carry_Out, OPCODE, out, Less, set);
  output [3:0] set;
  input [3:0] a,b,Less;
  input Carry_In;
  input [2:0] OPCODE;
  output [3:0] out;
  output Carry_Out;
  wire [3:0] AND, OR, SUM;
  wire binvert;
  reg [3:0] temp_b;

  assign binvert = OPCODE[2];
  always @*
  begin
    temp_b = b;
    if (binvert == 1'b1)
      temp_b = ~b;
    end
    assign AND = a & temp_b;
    assign OR = a | temp_b;
    ripple_adder_LA f0(a, temp_b, Carry_In, Carry_Out, SUM);

    mux4 f1(AND[0], OR[0], SUM[0], Less[0], OPCODE[1:0], out[0]);
    mux4 f2(AND[1], OR[1], SUM[1], Less[1], OPCODE[1:0], out[1]);

```

Oct 15, 10 13:25

alu\_design.v

Page 3/5

```

mux4 f3(AND[2], OR[2], SUM[2], Less[2], OPCODE[1:0], out[2]);
mux4 f4(AND[3], OR[3], SUM[3], Less[3], OPCODE[1:0], out[3]);
assign set[3:1] = 3'b000;
assign set[0] = SUM[3];
endmodule

module ALU16_CLA(a, b, OPCODE, out, Zero, Overflow);
input [15:0] a, b;
input [2:0] OPCODE;
output [15:0] out;
output Zero, Overflow;
wire [3:0] Carry;
wire [3:0] set;
reg overflow_temp = 1'b0;

ALU_slice_CLA f0(a[3:0], b[3:0], OPCODE[2], Carry[0], OPCODE, out[3:0], set);
ALU_slice_CLA f1(a[7:4], b[7:4], Carry[0], Carry[1], OPCODE, out[7:4], 4'b0000);
ALU_slice_CLA f2(a[11:8], b[11:8], Carry[1], Carry[2], OPCODE, out[11:8], 4'b0000);
ALU_slice_CLA_MSB f3(a[15:12], b[15:12], Carry[2], Carry[3], OPCODE, out[15:12], 4'b0000, set);

assign Zero = (out==16'h0000);

always @*
if(OPCODE[2:1] == 2'b01)
begin
if(a[15]==1 && b[15]==1 && out[15]!=1)
overflow_temp = 1'b1;
else if(a[15]==0 && b[15]==0 && out[15]!=0)
overflow_temp = 1'b1;
end;

always @*
if(OPCODE[2:1] == 2'b11)
begin
if(a[15]==1 && b[15]==0 && out[15]!=1)
overflow_temp = 1'b1;
else if(a[15]==0 && b[15]==1 && out[15]!=0)
overflow_temp = 1'b1;
end;

assign Overflow = overflow_temp;
endmodule

//4-to-1 MUX://
module mux4(a, b, c, d, s, out);
input a,b,c,d;
input [1:0] s;
output out;
reg out;

always@(a or b or c or d or s)
case (s)
0: out=a;
1: out=b;
2: out=c;
3: out=d;
default: $display("Error in selection");
endcase
endmodule

//CLA Adder Modules://
module ripple_adder_LA(a, b, cin, cout, sum);
input [3:0] a, b;
input cin;
output cout;

```

Oct 15, 10 13:25

alu\_design.v

Page 4/5

```

output [3:0] sum;
wire [4:0] c; // used for carry connections
wire [3:0] g;
wire [3:0] p;
wire P,G;
assign c[0]=cin;
fulladder_LA f0(a[0], b[0], c[0], sum[0], p[0], g[0]);
fulladder_LA f1(a[1], b[1], c[1], sum[1], p[1], g[1]);
fulladder_LA f2(a[2], b[2], c[2], sum[2], p[2], g[2]);
fulladder_LA f3(a[3], b[3], c[3], sum[3], p[3], g[3]);

lookahead f4(p[3],p[2],p[1],p[0],g[3],g[2],g[1],g[0],c[0],c[1],c[2],c[3],c[4],P,G);
assign cout = c[4];
endmodule

module fulladder_LA(a, b, cin, sum, p, g);
input a, b, cin;
output sum, p, g;
assign sum = a ^ b ^ cin;
assign p = a | b;
assign g = a & b;
endmodule

module lookahead(p3,p2,p1,p0,g3,g2,g1,g0,c0,c1,c2,c3,c4,P,G);
input p3,p2,p1,p0,g3,g2,g1,g0,c0;
output c1,c2,c3,c4,P,G;

assign c4 = g3 | (p3 & g2) | (p3 & p2 & g1) | (p3 & p2 & p1 & g0) | (p3 & p2 & p1 & p0 & c0);
assign c3 = g2 | (p2 & g1) | (p2 & p1 & g0) | (p2 & p1 & p0 & c0);
assign c2 = g1 | (p1 & g0) | (p1 & p0 & c0);
assign c1 = g0 | (p0 & c0);
assign P = p3 & p2 & p1 & p0;
assign G = g3 & g2 & g1 & g0;
endmodule

//Ripple/Fulladder Modules://
module fulladder(a, b, cin, sum, cout);
input a, b, cin;
output sum, cout;
assign sum = a ^ b ^ cin;
assign cout = a & b | a & cin | b & cin;
endmodule

module ripple_adder(a, b, sum, cout);
input [15:0] a, b;
output [15:0] sum;
output cout;
wire [15:0] c; // used for carry connections
assign c[0]=0;

fulladder f0(a[0], b[0], c[0], sum[0], c[1]);
fulladder f1(a[1], b[1], c[1], sum[1], c[2]);
fulladder f2(a[2], b[2], c[2], sum[2], c[3]);
fulladder f3(a[3], b[3], c[3], sum[3], c[4]);
fulladder f4(a[4], b[4], c[4], sum[4], c[5]);
fulladder f5(a[5], b[5], c[5], sum[5], c[6]);
fulladder f6(a[6], b[6], c[6], sum[6], c[7]);
fulladder f7(a[7], b[7], c[7], sum[7], c[8]);
fulladder f8(a[8], b[8], c[8], sum[8], c[9]);
fulladder f9(a[9], b[9], c[9], sum[9], c[10]);
fulladder f10(a[10], b[10], c[10], sum[10], c[11]);
fulladder f11(a[11], b[11], c[11], sum[11], c[12]);
fulladder f12(a[12], b[12], c[12], sum[12], c[13]);
fulladder f13(a[13], b[13], c[13], sum[13], c[14]);
fulladder f14(a[14], b[14], c[14], sum[14], c[15]);

```

Oct 15, 10 13:25

alu\_design.v

Page 5/5

```
    fulladder f15(a[15], b[15], c[15], sum[15], cout);  
endmodule
```